 


## Part A: FSM State Diagram



FSM State Table for Gate Control System

| Current State | Input A | Input B | New State |
|---------------|---------|---------|-----------|
| Lowered       | 0       | 1       | Lowered   |
| Lowered       | 1       | 1       | Raising   |
| Raising       | x       | 0       | Raising   |
| Raising       | x       | 1       | Raised    |
| Raised        | 0       | 1       | Lowering  |
| Raised        | 1       | 1       | Raised    |
| Lowering      | 0       | 0       | Lowering  |
| Lowering      | 1       | 0       | Raising   |
| Lowering      | x       | 1       | Lowered   |

### FSM State Table with Flip-Flop Assignments and Ouput

| State |    | Input |   | NextState |       |          | Output |   |
|-------|----|-------|---|-----------|-------|----------|--------|---|
| F1    | F0 | A     | B | NewF1     | NewF0 | State    | R      | L |
| 0     | 0  | 0     | 1 | 0         | 0     | Lowered  | 0      | 0 |
| 0     | 0  | 1     | 1 | 0         | 1     | Raising  | 1      | 0 |
| 0     | 1  | x     | 0 | 0         | 1     | Raising  | 1      | 0 |
| 0     | 1  | x     | 1 | 1         | 0     | Raised   | 0      | 0 |
| 1     | 0  | 0     | 1 | 1         | 1     | Lowering | 0      | 1 |
| 1     | 0  | 1     | 1 | 1         | 0     | Raised   | 0      | 0 |
| 1     | 1  | 0     | 0 | 1         | 1     | Lowering | 0      | 1 |
| 1     | 1  | 0     | 1 | 0         | 0     | Lowered  | 0      | 0 |
| 1     | 1  | 1     | 0 | 0         | 1     | Raising  | 1      | 0 |

### Complete truth table

| $F1F0[1..0]$ |   | A | B | $NewF1NewF0[1..0]$ |   | R | L |
|--------------|---|---|---|--------------------|---|---|---|
| 0            | 0 | 0 | 0 | 0                  | 1 | 1 | 0 |
| 0            | 0 | 0 | 1 | 0                  | 0 | 0 | 0 |
| 0            | 0 | 1 | 0 | 0                  | 1 | 1 | 0 |
| 0            | 0 | 1 | 1 | 0                  | 1 | 1 | 0 |
| 0            | 1 | 0 | 0 | 0                  | 1 | 1 | 0 |
| 0            | 1 | 0 | 1 | 1                  | 0 | 0 | 0 |
| 0            | 1 | 1 | 0 | 0                  | 1 | 1 | 0 |
| 0            | 1 | 1 | 1 | 1                  | 0 | 0 | 0 |
| 1            | 0 | 0 | 0 | 1                  | 1 | 0 | 1 |
| 1            | 0 | 0 | 1 | 1                  | 1 | 0 | 1 |
| 1            | 0 | 1 | 0 | 1                  | 1 | 1 | 0 |
| 1            | 0 | 1 | 1 | 1                  | 0 | 0 | 0 |
| 1            | 1 | 0 | 0 | 1                  | 1 | 0 | 1 |
| 1            | 1 | 0 | 1 | 0                  | 0 | 0 | 0 |
| 1            | 1 | 1 | 0 | 0                  | 1 | 1 | 0 |
| 1            | 1 | 1 | 1 | 0                  | 0 | 0 | 0 |

This is a Mealy machine since its output depends on both current state and current input.

## Part B

Table 1: Full State Transition Table with Inputs and Outputs

| Step | R1mul | R1en | R2mul | R2en | InSel | ASel | BSel | Done | NextStep |
|------|-------|------|-------|------|-------|------|------|------|----------|
| 000  | 0     | 1    | x     | 0    | 01    | 11   | 00   | 0    | 001      |
| 001  | 1     | 1    | 0     | 0    | 00    | 11   | 01   | 0    | 010      |
| 010  | 1     | 1    | 0     | 0    | 00    | 11   | 01   | 0    | 011      |
| 011  | x     | 0    | 0     | 1    | 10    | 11   | 00   | 0    | 100      |
| 100  | x     | 0    | 1     | 1    | 00    | 11   | 10   | 0    | 101      |
| 101  | 0     | 1    | x     | 0    | xx    | 10   | 01   | 0    | 110      |
| 110  | 0     | 1    | x     | 0    | 11    | 11   | 01   | 0    | 111      |
| 111  | 0     | 0    | x     | 0    | xx    | xx   | xx   | 1    | 111      |